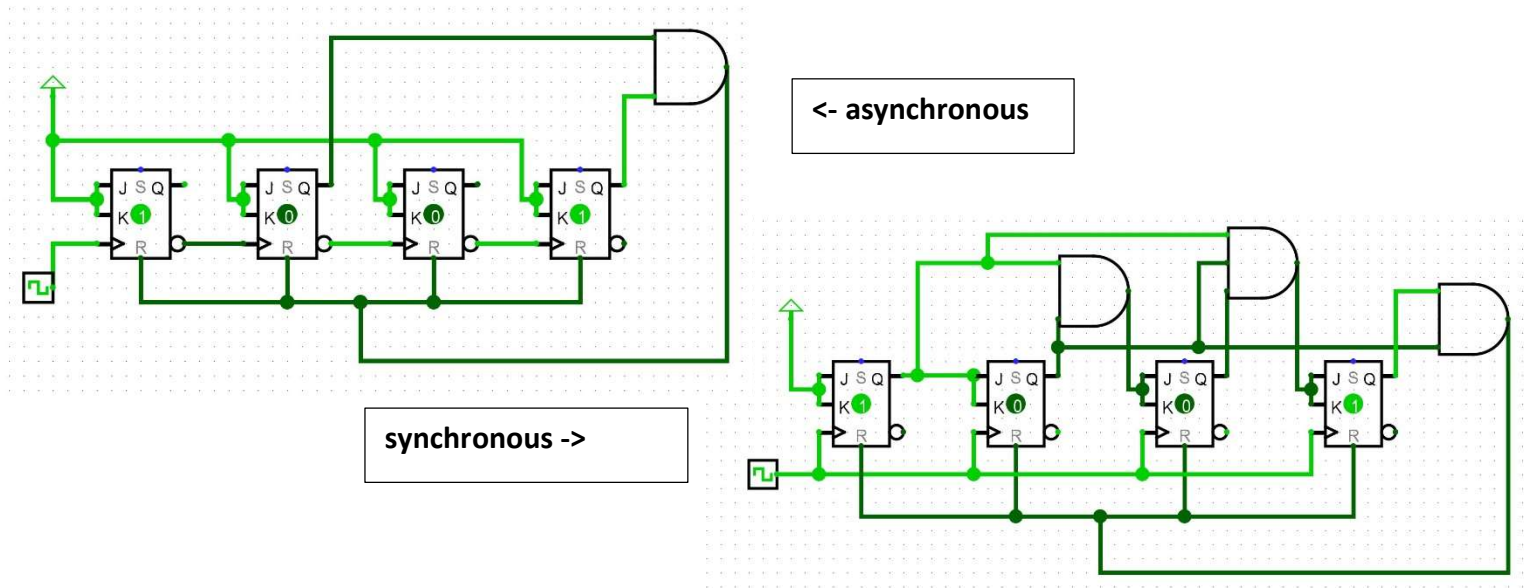


Problem A: Mod-10 synchronous JK counter

Construct a mod-10 (counts up to decimal 9 / binary 1001, then loops back to 0) counter) using JK flip flops. ~~It must be synchronous — no glitch states!~~ Use JK in “toggle” mode. The below configuration has been provided for you as a starting point.



Problem B: Custom synchronous 3-bit counter

Given this state table, construct a **synchronous custom counter** using **D-type flip flops**. Hint: Construct Karnaugh maps by filling in where D_c , D_b , and D_a are 0, 1 or x respectively.

Note: None of the t_n states of the counter have a t_{n+1} state of 010 or 110. However, if the counter were to ever enter those states (say, a random glitch happened), it should return to the sequence and not get stuck in those states.

t_n						t_{n+1}		
Q_c	Q_b	Q_a	D_c	D_b	D_a	Q_c	Q_b	Q_a
0	0	1	1	0	0	1	0	0
1	0	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0
0	0	0	0	1	1	0	1	1
0	1	1	1	0	1	1	0	1
1	0	1	0	0	1	0	0	1
0	1	0	x	x	x	x	x	x
1	1	0	x	x	x	x	x	x

Dc

Qc\QbQa	00	01	11	10
0	0	1	1	x
1	1	0	0	x

$$\neg QcQa + Qc\neg Qa$$

$$Qc \text{ XOR } Qa$$

Db

Qc\QbQa	00	01	11	10
0	1	0	0	x
1	1	0	0	x

$$\neg Qb\neg Qa + Qb\neg Qa$$

$$= \neg Qa$$

Da

Qc\QbQa	00	01	11	10
0	1	0	1	x
1	1	1	0	x

$$\neg Qa + \neg QcQb + Qc\neg Qb$$

$$\neg Qa + Qc \text{ XOR } Qb$$

